

Question 1

assume cut-off

$$I_D = 0 \rightarrow V_{GS} = 5V > V_T$$

not cut-off

assume saturation

$$I_D = \frac{1}{2} k_n' \frac{W}{L} (V_{GS} - V_T)^2$$

$$I_D = \frac{1}{2} \cdot 1 \cdot (V_{GS} - 1)^2$$

$$V_{GS} = V_{DS} = 5V - 1k \cdot I_D$$

$$5 - V_{DS} = \frac{1}{2} (V_{DS} - 1)^2$$


$$10 - 2V_{DS} = V_{DS}^2 - 2V_{DS} + 1$$

$$V_{DS}^2 = 9$$

$$V_{DS} = \pm 3, \text{ but } -3V \text{ is unphysical}$$

$$\boxed{V_0 = 3V}$$

$V_{DS} = V_{GS} > V_{GS} - V_T \rightarrow$ transistor must be in
saturation mode

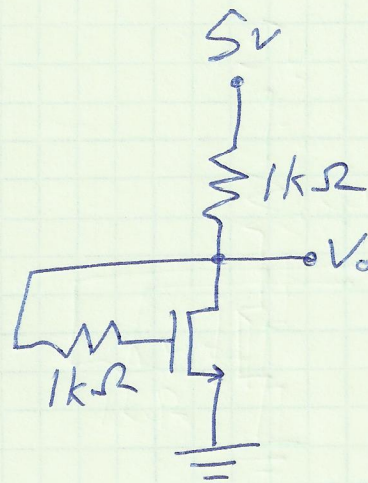

Question 2

assume cut-off

$$I_B = 0, I_C = 0 \rightarrow V_{EB} = 1V > V_{D0}$$

not in cut-off

assume active

$$1V - 1k \cdot (\beta + 1) I_B - 0.7V - 10k \cdot I_B = 0$$

$$0.3V - 111k I_B = 0$$

$$I_B = \frac{0.3V}{111k} = 2.7\mu A$$

$$I_C = \beta I_B = 0.27mA$$


$$1V - 1k \cdot 0.27mA - V_{EC} - 1k \cdot 0.27mA + 1V = 0$$

$$2 - 2 \cdot 0.27 = V_{EC} = 1.46V > V_{D0}$$

→ transistor is in active mode

$$V_o = -1V + 1k \cdot 0.27mA$$

$$V_o = -0.73V$$

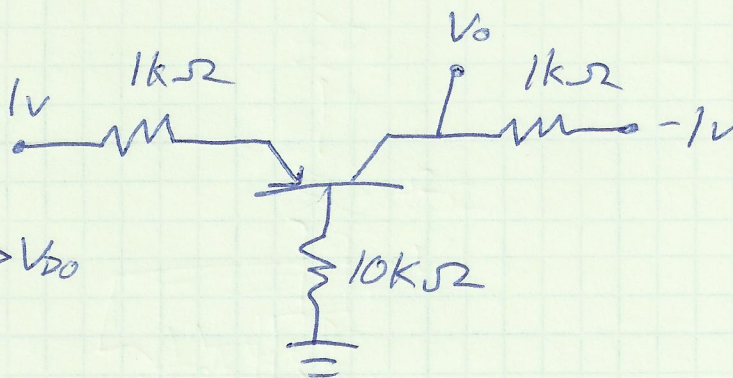

Question 3

$$V_G = \frac{5}{2} = 2.5V$$

$$V_{SG} = 5 - 2.5 = 2.5V > |V_T|$$

transistor not in cut-off

assume saturation

$$I_D = \frac{1}{2} k_p' \frac{W}{L} (V_{SG} - |V_T|)^2$$

$$I_D = \frac{1}{2} \cdot 1mA \cdot (2.5 - 1)^2 = 1.1mA$$

$$V_{SD} = 5V - 10k \cdot 1.1mA = 5 - 11 = -6V \rightarrow \text{unphysical}$$

transistor not in saturation

assume triode

$$I_D = \frac{1}{2} k_p' \frac{W}{L} [2V_{SD}(V_{SG} - |V_T|) - V_{SD}^2]$$

$$5V - V_{SD} - 10k \cdot I_D = 0$$

$$\frac{5 - V_{SD}}{10} = \frac{1}{2} \cdot 1 \cdot [2V_{SD} \cdot 1.5 - V_{SD}^2]$$

$$10 - 2V_{SD} = 30V_{SD} - 10V_{SD}^2$$

$$10V_{SD}^2 - 32V_{SD} + 10 = 0$$


$$V_{SD} = \frac{32 \pm \sqrt{32^2 - 400}}{20} = 0.35V \text{ or } 2.85V$$

unphysical
↓

$$V_O = 5V - 0.35V$$

$$\boxed{V_O = 4.65V}$$


transistor is in triode mode because
we have ruled out cut-off and saturation

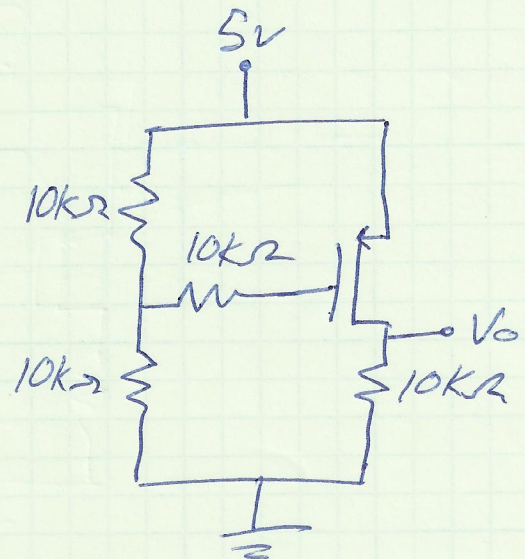

Question 4

cut-off for both transistors is unlikely because if $i_{B1} = 0, i_{B2} = 0$, then $V_{BE1} + V_{BE2} = 5V > V_{DD}$

assume Q_1 and Q_2 active

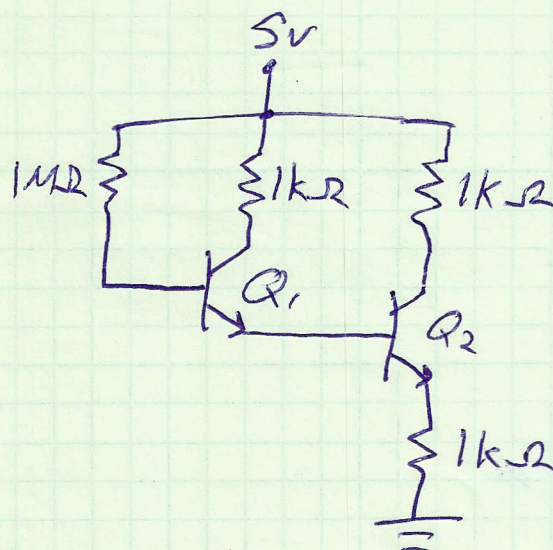

$$5 - 1M \cdot i_{B1} - 0.7 - 0.7 - 1k \cdot i_{C2} = 0, \quad i_{C2} = \beta i_{B2} = \beta i_{C1} = \beta^2 i_{B1}$$

$$5 - 1M i_{B1} - 1.4 - 1k \cdot \beta^2 i_{B1} = 0$$

$$i_{B1} = \frac{5 - 1.4}{1M} = 0.33 \mu A$$

$$i_{C1} = \beta i_{B1} = 33 \mu A = i_{B2}$$

$$i_{C2} = \beta i_{B2} = 3.3 mA$$

$$V_{CE2} = 5 - 1k \cdot 3.3 mA - 1k \cdot 3.3 mA = -1.6V \rightarrow \text{unphysical}$$

assume Q_2 in saturation

$$i_{C2} = \frac{5V - 0.2V}{2k} = 2.4 mA$$

$$V_{E2} = 1k \cdot 2.4 mA = 2.4V$$

$$V_D = V_{E2} + V_{CE2} = 2.4V + 0.2V$$

$$V_{E1} = V_{E2} + V_{D0} = 2.4V + 0.2V$$

$$\boxed{V_D = 2.6V}$$

$$V_{E1} = 3.1V$$

$$i_{B1} = \frac{5V - 0.2V - 3.1V}{1M} = 1.2 \mu A, \quad i_{C1} = \beta i_{B1} = 120 \mu A$$

$$V_{CE1} = 5V - 3.1V - 1k \cdot 120 \mu A = 1.78V > V_{D0}$$

so Q_1 is in active mode

$$\frac{i_{C2}}{i_{B2}} = \frac{2.4 mA}{120 \mu A} = 20 < \beta \text{ so } Q_2 \text{ is in } \underline{\text{saturation mode}}$$