

ECE 45 DC Circuits Review

Circuits Concepts:

- *Sources*: voltages in series can be combined; currents in parallel can be combined.


The power supplied/dissipated by a component is the current multiplied by the voltage drop. If current flows from higher to lower (lower to higher) voltage, power is dissipated (supplied).

- A *branch* is two components (source, resistor, capacitor, inductor, etc.) connected end to end.
- A *node* is a connection of multiple branches.


Nodes have a particular voltage, and branches have a particular current.

- **Kirchhoff's Current Law**: A node has zero net current, i.e. the incoming current of a node equals the outgoing current of a node.
- **Kirchhoff's Voltage Law**: The net voltage in a closed loop in a circuit is zero.
- These laws can be used to set up systems of equations which can be used to solve for specific voltages and currents in the circuit.
- **KCL (Node Voltage)**: (Used by SPICE)
 - Assign a node to be the reference ground, 0V.
 - Assign a voltage V_i to all additional nodes, where V_i is the voltage with respect to ground.
 - Decide on arbitrary directions for the currents in each branch. It helps to write equations for each current in terms of the voltages V_i ahead of time for consistency.
 - For each node, the net current is zero, so write an equation $\sum I_{in} = \sum I_{out}$.
 - Solve the system of equations for desired values.
- **KVL (Mesh Current)**: (Generally easier if fewer loops than nodes.)
 - Assign each independent loop a current I_i .
 - Write a KVL equation for each loop such that $\sum V = 0$. It helps to write equations for each voltage in terms of the currents I_i ahead of time.
 - If multiple loops include a branch, the current in that branch is the sum of the loops which include that branch.
 - Solve the system of equations.
- **Power**: The power generated or dissipated by a component is proportionate to the current through the component and the voltage across the component. $P = VI$.

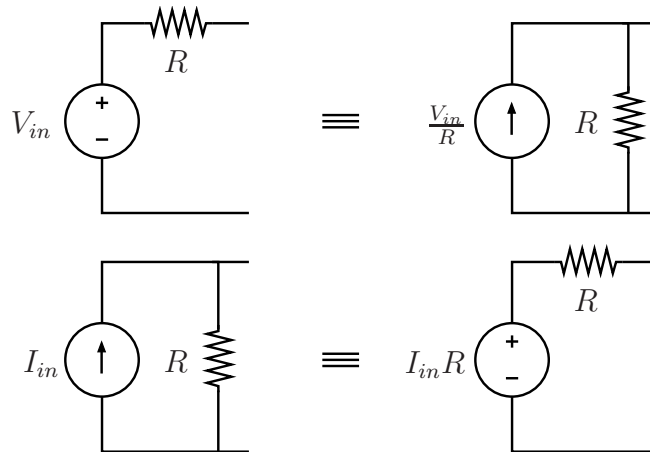- **Source Transformation:** Replace a current/voltage source with a voltage/current source:



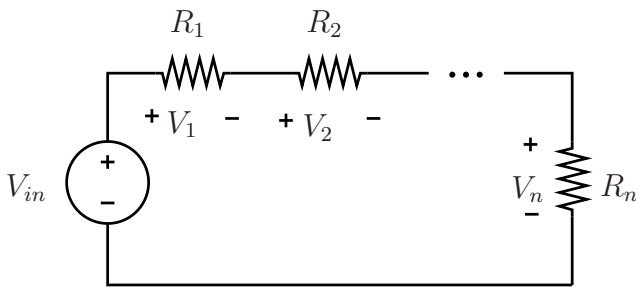
- **Voltage/Current Divider:** Application of KCL/KVL that allows for quick calculation of a voltage/current. For any $n \geq 2$.



Voltage Divider:

$$V_k = V_{in} \frac{R_k}{R_1 + R_2 + \dots + R_n}$$

for each $k = 1, 2, \dots, n$

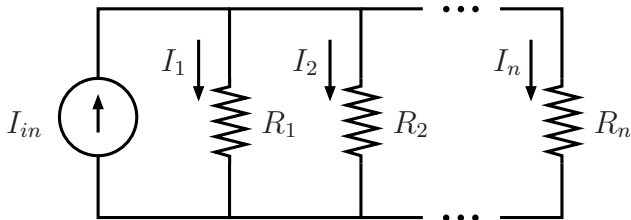


Current Divider:

$$I_k = I_{in} \frac{\frac{1}{R_k}}{\frac{1}{R_1} + \frac{1}{R_2} + \dots + \frac{1}{R_n}}$$

for each $k = 1, 2, \dots, n$

Circuit Examples:

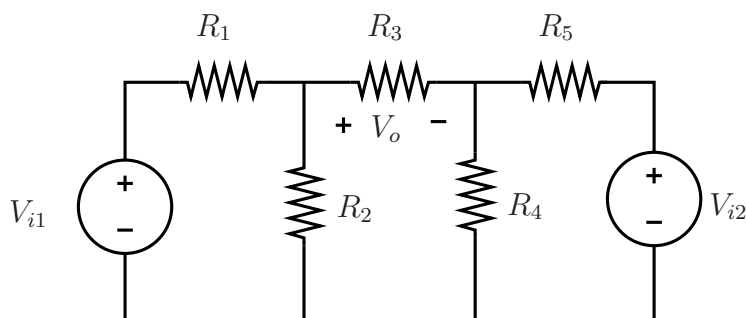1. Find the output voltage of the following circuit:



$$V_{i1} = 20V$$


$$V_{i2} = 5V$$

$$R_1 = R_2 = R_5 = 10\Omega$$

$$R_3 = R_4 = 5\Omega$$

Solutions

Labeling currents and voltages gives us:

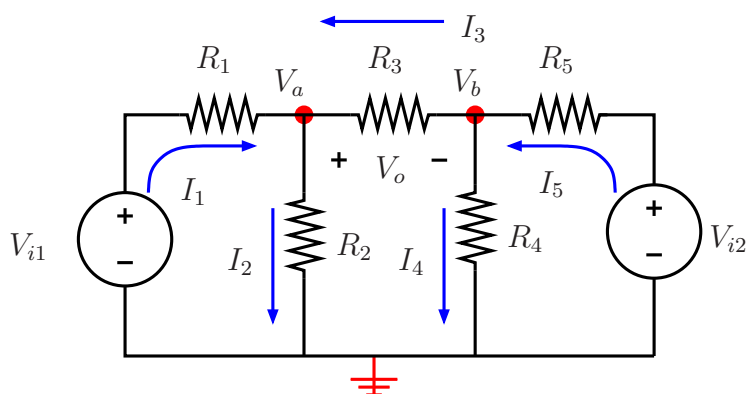

By KCL:

$$\sum I_{in} = \sum I_{out}$$

$$a) I_1 + I_3 = I_2$$

$$b) I_5 = I_3 + I_4$$

By Ohm's Law:

$$I_1 = (V_{i1} - V_a)/R_1$$

$$I_2 = V_a/R_2$$

$$I_3 = (V_b - V_a)/R_3$$

$$I_4 = V_b/R_4$$

$$I_5 = (V_{i2} - V_b)/R_5$$

Substituting expressions for I_1, \dots, I_5 into a) and b) gives us:

$$a) \quad \frac{V_{i1}}{R_1} = V_a \left(\frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3} \right) - V_b \frac{1}{R_3}$$

$$b) \quad \frac{-V_{i2}}{R_5} = V_a \frac{1}{R_3} - V_b \left(\frac{1}{R_3} + \frac{1}{R_4} + \frac{1}{R_5} \right)$$


Plugging in numerical values and subtracting a) from b) gives us

$$V_b \frac{4}{5} = 3 \rightarrow V_b = \frac{15}{4} V \text{ and } V_a = \frac{55}{8} V$$

and so

$$V_o = V_a - V_b = \frac{25}{8} V$$


2. Find the power dissipated by R_6

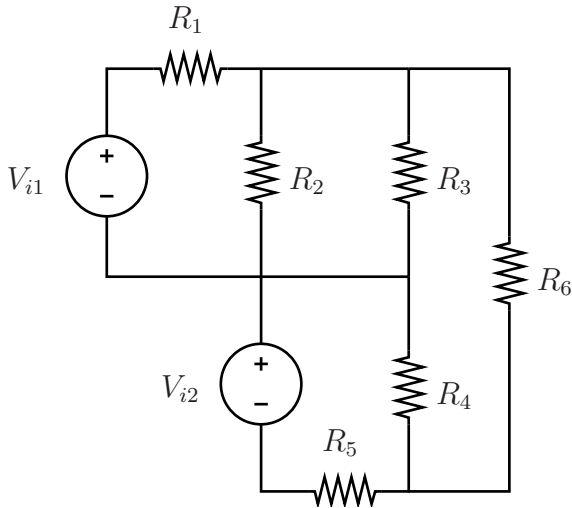

$$\begin{aligned} V_1 &= 1V \\ V_2 &= 2V \\ R_1 &= R_4 = 2\Omega \\ R_2 &= 1\Omega \\ R_3 &= R_5 = 4\Omega \\ R_6 &= 8\Omega \end{aligned}$$

Solutions

Labeling currents and voltages gives us:

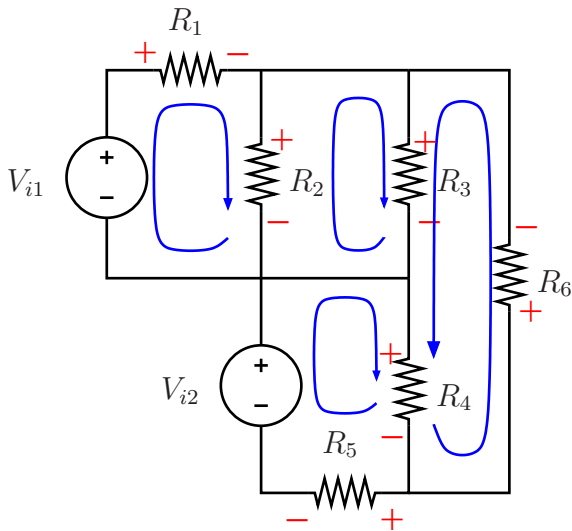

By KVL:

$$\sum V_{gain} = \sum V_{drop}$$

$$1) V_1 = V_{R1} + V_{R2}$$

$$2) V_{R2} = V_{R3}$$

$$3) V_2 = V_{R4} + V_{R5}$$

$$4) 0 = V_{R3} + V_{R4} + V_{R6}$$

By Ohm's Law:

$$V_{R1} = R_1 I_1$$

$$V_{R2} = R_2 (I_1 - I_2)$$

$$V_{R3} = R_3 (I_2 + I_4)$$

$$V_{R4} = R_4 (I_3 + I_4)$$

$$V_{R5} = R_5 I_3$$

$$V_{R6} = R_6 I_4$$

Plugging in numerical values and substituting the expressions for V_{R1}, \dots, V_{R6} into 1), ..., 4) yields:

$$\begin{aligned} 1) \quad 1 &= 3 I_1 - I_2 \\ 2) \quad 0 &= I_1 - 5 I_2 - 4 I_4 \\ 3) \quad 2 &= 6 I_3 + 2 I_4 \\ 4) \quad 0 &= 4 I_2 + 2 I_3 + 14 I_4 \end{aligned} \rightarrow \begin{pmatrix} 3 & -1 & 0 & 0 \\ 1 & -5 & 0 & -4 \\ 0 & 0 & 6 & 2 \\ 0 & 4 & 2 & 14 \end{pmatrix} \begin{pmatrix} I_1 \\ I_2 \\ I_3 \\ I_4 \end{pmatrix} = \begin{pmatrix} 1 \\ 0 \\ 2 \\ 0 \end{pmatrix} \rightarrow \begin{aligned} I_1 &= 5/13A \\ I_2 &= -2/13A \\ I_3 &= 19/52A \\ I_4 &= -5/52A \end{aligned}$$

Now that we know the values of all of the currents in the circuit, we can solve for the current through R_6 and the voltage across R_6 , and so:

$$P_{R6} = V_{R6} I_{R6} = R_6 (I_{R6})^2 = \frac{25}{338} W$$