

PHASOR METHOD

The phasor method can be applied to find the response of a circuit to sinusoidal excitation (AC analysis)

It is based on the following steps:

- ① Write the input in the form $A \cos(\omega t + \phi)$
- ② Write the corresponding phasor $A e^{j\phi}$
- ③ Change circuit components into impedances

$$R \rightarrow R$$

$$C \rightarrow 1/j\omega C$$


$$L \rightarrow j\omega L$$
- ④ Solve impedance circuit as it was a resistor network
- ⑤ Write the phasor of the solution $B e^{j\phi}$ (Response in PHASOR Domain)
- ⑥ Multiply by $e^{j\omega t}$
- ⑦ Take the real part (Response in Time domain)

NOTE: For step ① if instead then $\cos(\omega t + \phi)$ you have $\sin(\omega t + \phi)$ what do you do?

Remember $\sin(\omega t + \phi) = \cos(\omega t + \phi - \pi/2)$

How about you have two sinusoids?

We'll see this with an example.

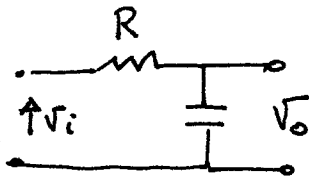

Consider a simple RC circuit where the input is V_i and the output is V_o

Using phasors we can write the following response:

$$V_o = \frac{Z_c}{Z_R + Z_c} V_i = \frac{1/j\omega C}{R + 1/j\omega C} V_i = \frac{1}{1 + j\omega RC} V_i$$

We call:

$$H(\omega) = \frac{1}{1 + j\omega RC}$$

This is an important quantity.

It gives the response to an excitation at a given frequency ω .

Assume now the input is given by two sinusoids:

$$V_i(t) = \frac{4}{\pi} \sin(8\pi t) + \frac{2}{\pi} \sin(16\pi t)$$

We can use the principle of superposition and solve separately for the two frequencies and then add the results. Let $\omega_1 = 8\pi$, $\omega_2 = 16\pi$

$$V_1 = \frac{4}{\pi} e^{j0} e^{-j\pi/2}$$

$$\text{phasor for } V_1 = \frac{4}{\pi} \sin(8\pi t)$$

$$V_2 = \frac{2}{\pi} e^{j0} e^{-j\pi/2}$$

$$\text{phasor for } V_2 = \frac{2}{\pi} \sin(16\pi t)$$

$$H(\omega_1) = \frac{1}{1 + j8\pi RC}$$

$$H(\omega_2) = \frac{1}{1 + j16\pi RC}$$

$$\text{Response to } V_1: V_o^{(1)} = \frac{1}{1 + j8\pi RC} \frac{4}{\pi} e^{-j\pi/2} = |H(\omega_1)| \frac{4}{\pi} e^{j\angle H(\omega_1) - j\pi/2}$$


$$\text{Response to } V_2: V_o^{(2)} = \frac{1}{1 + j16\pi RC} \frac{2}{\pi} e^{-j\pi/2} = |H(\omega_2)| \frac{2}{\pi} e^{j\angle H(\omega_2) - j\pi/2}$$

We now go back to time domain multiplying by $e^{j\omega t}$ and taking the real part.

$$\begin{aligned} & \operatorname{Re}[V_0^{(1)} e^{j8\pi t}] + \operatorname{Re}[V_0^{(2)} e^{j16\pi t}] \\ &= \frac{4}{\pi} |H(8\pi)| \sin(8\pi t + \angle H(8\pi)) + \frac{2}{\pi} |H(16\pi)| \sin(16\pi t + \angle H(16\pi)) \end{aligned}$$


Notice that each sinusoid undergoes a phase shift given by the phase of H at the given frequency and is multiplied by the amplitude of H at the given frequency

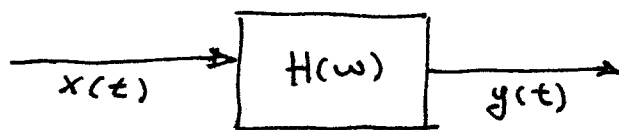The response function obtained writing $\frac{\text{output}}{\text{input}}$ in phasor domain is quite important as it tells us the attenuation and phase shift of ~~any~~ a sinusoid of any given frequency. We can represent this in abstract terms as a system of input $x(t)$ output $y(t)$



in The previous case $x(t)$ was ~~imp~~ voltage V_i and $y(t)$ was voltage V_o on capacitor.

$H(\omega)$ is the response To a sinusoid of frequency ω .
Suppose $|H(\omega)| < 1$ it means The sinusoid is attenuated by the system.

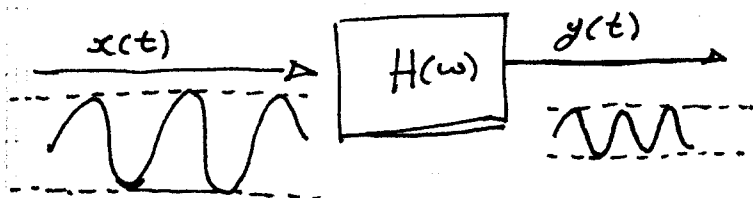

Attenuated by how much?


It depends on the frequency of the sinusoid and on the function $H(\omega)$.

For example:

$$V_o = V_i \frac{1}{1+j\omega RC}$$

$$\begin{aligned} \omega \rightarrow 0 \quad V_o &= V_i \\ \omega \rightarrow \infty \quad V_o &= 0 \end{aligned}$$



$$|H(\omega)| = \frac{1}{\sqrt{1+(\omega RC)^2}} e^{-j \arctan \omega RC}$$

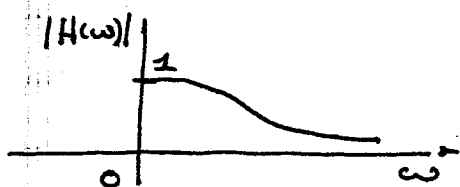

This shows that high frequency sinusoids are attenuated and low frequency sinusoids are not.

Since it attenuates only high frequencies, it is called Low-PASS filter.

Consider instead:

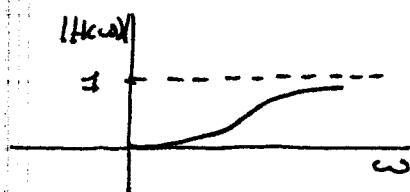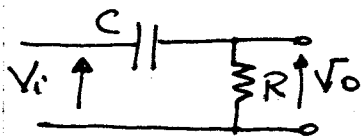

$$V_o = V_i \frac{R}{R + \frac{1}{j\omega C}}$$


$$\begin{aligned} \omega \rightarrow \infty \quad V_o &= V_i \\ \omega \rightarrow 0 \quad V_o &= 0 \end{aligned}$$

$$\begin{aligned} &= \frac{j\omega C R}{1 + j\omega C R} V_i \\ &= \frac{\omega C R}{\sqrt{1 + (\omega C R)^2}} e^{j(\frac{\pi}{2} - \arctan \omega C R)} \end{aligned}$$

HIGH-PASS filter

because it attenuates only the low frequencies

(5)

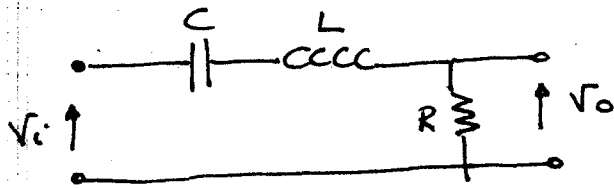BAND-PASS filter


$$V_o = V_i \frac{R}{R + \frac{1}{j\omega C} + j\omega L} = \frac{j\omega CR}{j\omega CR + 1 + (j\omega)^2 LC} V_i$$

$$\omega = \sqrt{\frac{1}{LC}} \quad |H(\omega)| = 1$$

$$\omega \rightarrow \infty \quad |H(\omega)| = 0$$

$$\omega \rightarrow 0 \quad |H(\omega)| = 0$$

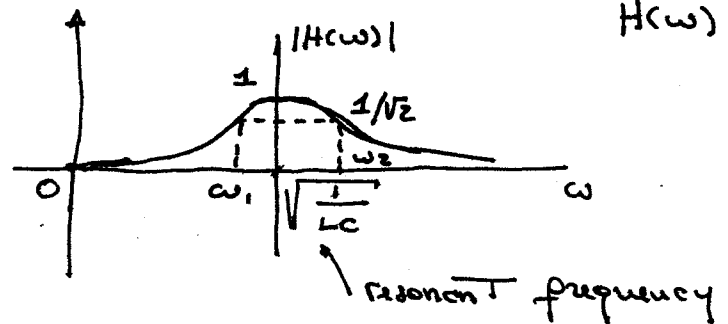$\omega_2 - \omega_1$ is the BAND of the filter



$$Q = \frac{1}{R} \sqrt{\frac{L}{C}} \text{ is the quality factor of the filter.}$$

Q increases the sharper is the resonance effect and the filter becomes more frequency selective



How about the phase?

Remember that

① Any complex number is characterized by magnitude AND phase

② Response $H = \underbrace{|H|}_{\text{multiplication factor for amplitude sinusoid at the input}} e^{j\phi}$

multiplication factor for amplitude sinusoid at the input


phase factor to be added to the sinusoid

LOW PASS FILTER

We have seen $H = \frac{V_o}{V_i} = \frac{1}{\sqrt{1 + (\omega RC)^2}}$

$-j \arctan \omega RC$

The phase plot is $-\arctan \omega RC$

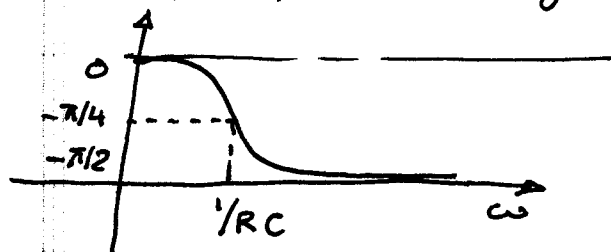


Gives a negative shift in frequency to the applied sinusoid

HIGH PASS FILTER

We have seen $H = \frac{V_o}{V_i} = \frac{\omega RC}{\sqrt{1 + (\omega RC)^2}}$

$+ (-j \arctan \omega RC + \pi/2)$

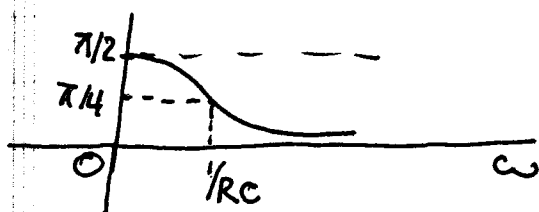

Gives a positive shift in frequency to the applied sinusoid